

(32.1)

$$\underbrace{\mu_0 \vec{j}(t) = \text{curl} \vec{B}(t)}_{\substack{\text{Ampere's law:} \\ \text{A time varying current creates } \vec{B}(t)}} \Rightarrow \underbrace{\frac{\partial \vec{B}}{\partial t} = -\text{curl} \vec{E}_L}_{\substack{\text{Faraday's law: A time varying magnetic field} \\ \text{creates an induced (back) emf in the same loop.}}$$

$$\mu_0 I(t) = \oint_{\text{loop } l} \vec{B}(t) \cdot d\vec{s} = Bl \Rightarrow B(t) = \frac{\mu_0 I(t)}{l} \quad \text{Now use Faraday's law with this B:}$$

$$\Rightarrow \frac{d\Phi_B}{dt} = -\varepsilon(t) \Rightarrow$$

$$\varepsilon_L = -\frac{d\Phi_B}{dt} = -\frac{d}{dt} \left(\frac{\mu_0 I(t)}{l} A \right) = - \underbrace{\frac{\mu_0}{l} A}_{\text{self-inductance } L} \cdot \frac{dI}{dt}$$

$$(32.2) \quad \varepsilon_L = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$$

$$(32.3) \quad L = \frac{N\Phi_B}{I}$$

$$(32.4) \quad \Delta V_R = -RI \quad \text{and} \quad \varepsilon_{\text{ind}} = \Delta V_L = -L \frac{dI}{dt}$$

$$(32.5) \quad L_{\text{solenoid}} = \mu_0 n^2 V \quad U_B = \frac{1}{2} LI^2 \quad u_E = \frac{1}{2} \varepsilon_0 E^2 \quad u_B = \frac{B^2}{2\mu_0}$$

$$(32.6) \quad \varepsilon_1 = -M \frac{dI_2}{dt} \quad \text{and} \quad \varepsilon_2 = -M \frac{dI_1}{dt}$$

Self inductance L:

1. A coil has an inductance of 3.00 mH, and the current in it changes from 0.200A to 1.50 A in 0.200s. Find the magnitude of the average induced emf in the coil during this time. -19.5 mV.
2. (3) A 10.0 mH inductor carries a current $I = I_{\text{max}} \sin \omega t$ with $I_{\text{max}}=5.00$ A and $f=60\text{Hz}$. What is the back emf as a function of time?
(18.8Vcos(377t))
3. (5) An inductor in the form of a solenoid contains 420 turns, is 16.0 cm in length, and has a cross-sectional area of 3.00cm^2 . What uniform rate of decrease of current through the inductor induces an emf of $175\text{E-}6$ V? (-0.422A/s)
4. (9) A self induced emf in a solenoid of inductance L changes in time as $\varepsilon = \varepsilon_0 e^{-kt}$. Find the total charge that passes through the solenoid, assuming the charge is finite. ($\frac{\varepsilon_0}{k^2 L}$).

RL circuits:

5. (11) A 12.0 Volt battery is connected into a series circuit containing a 10.0 Ohm resistor and a 2.00H inductor. How long will it take the current to reach 50% and 90% of its final value? (0.139s; 0.461s)
6. (17) An inductor has an inductance of 15.0 H and a resistance of 30.0 Ohm is connected across a 100-Volt battery. What is the rate of increase of the current at $t=0$ s and at $t=1.50$ s. (6.67A/s; 0.332 A/s)

Energy in a magnetic field:

7. Calculate the energy associated with the magnetic field of a 200 turn solenoid in which a current of 1.75A produces a flux of $3.70\text{E-}4$ Wb in each turn. (0.0648 J)
8. (25) On a clear day at a certain location, a 100V/m vertical electric field exists near the Earth's surface. At the same place, the Earth's magnetic field has a magnitude of $0.500\text{E-}4$ T. Compare the energy densities of the two fields. ($u_E = 44.2\text{n J/m}^3$; $u_B = 995\mu\text{J/m}^3$).
9. An RL circuit in which $L=4.00\text{H}$ and $R=5.00$ Ohms is connected to a 22.0 Volt battery at $t=0$. a) What energy is stored in the inductor when the current is 0.500A b) at what rate is energy being stored in the inductor when $I=1.00\text{A}$; c) What power is being delivered to the circuit by the battery when $I=0.500$ A?
(a) $U=0.500$ J b) 17.0 W; c) 11.0 W

Mutual Inductance:

10. (30) Two coils are close to each other. The first coil carries a time-varying current given by $I(t) = 5.00\text{A}e^{-0.0250t} \sin 377t$. At $t=0.800$ s, the emf measured across the second coil is -3.20 V. What is the mutual inductance of the coils? (1.73mH).

Oscillations in an LC-circuit:

11. (38) An LC-circuit consists of a 20 mH inductor and a $0.500\mu\text{F}$ capacitor. If the maximum instantaneous current is 0.100 A, what is the greatest potential difference across the capacitor? (20.0 V)
12. (41) A fixed inductance $L=1.05\text{E-}6$ H is used in series with a variable capacitor in the tuning section on a ship. What capacitance tunes the circuit to the signal from a transmitter broadcasting at 6.30MHz? (608 pF).
13. An LC-circuit (in series) with a open-close switch contains a 82.0 mH inductor and a $17.0\mu\text{F}$ capacitor that initially carries a charge of $180\mu\text{C}$. The switch is open for $t<0$ and then closed at $t=0$. a) Find the frequency in Hz of the resulting oscillations. At $t=1.00\text{ms}$, find b) the charge on the capacitor and c) the current in the circuit. a) 135Hz b) $119\mu\text{C}$ c)-114 mA.

RLC circuits:

14. (45) Consider an LC circuit in which $L=500\text{mH}$ and $C=0.100\mu\text{F}$ a) What is the resonance frequency ω_0 ; b) If a resistance of $1.00\text{k}\Omega$ is introduced into the circuit, what is the frequency of the damped oscillations c) What is the percent difference between the frequencies? a) $4.47\text{E}3$ /s; b) $4.36\text{E}3$ /s; c) 2.46%.